

## Tutorial 2


### Numerical on transistor

#### Topics:

- Simple transistor circuits analysis to apply KVL or KCL rules to estimate  $I_C$ ,  $I_B$ ,  $I_E$ ,  $\beta$ , and  $\alpha$  (using dc biasing – fixed bias, emitter bias and voltage divider)
- Simple transistor values to estimate  $I_C$ ,  $I_B$ ,  $I_E$ , leakage current, CE and CB voltage and current gain
- Q-point analysis

Below are the examples for the above topics. Please note that the exam questions will be modified. However, the analysis pattern would remain same. So, please practice more similar questions.

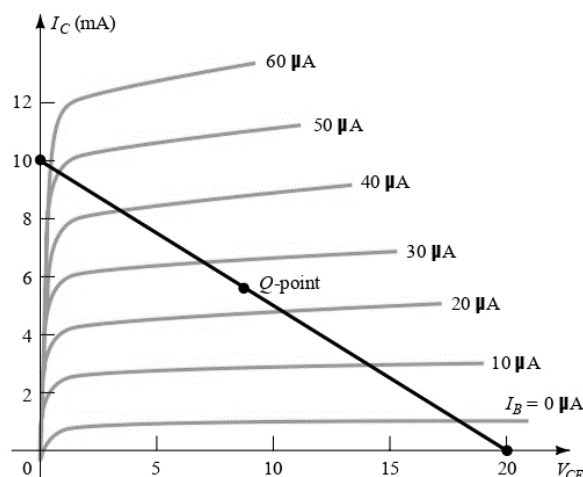- Given the load line of Figure and the defined Q-point, determine the required values of  $V_{CC}$ ,  $R_C$ , and  $R_B$  for a CE fixed-bias configuration.



**Answer:**  $V_{CC} = 20$  V (DC load line)

$$I_{C,sat} = 10 \text{ mA} = V_{CC} / R_C \text{ i.e. } R_C = 20 \text{ V} / 10 \text{ mA} = 2 \text{ k}\Omega$$

In CE configuration fixed bias,

$$V_{CC} - I_B R_B - V_{BE} = 0 \text{ (See the below figure)}$$

$$\text{i.e. } R_B = 20 - 0.7 / I_B$$

Please note, the  $V_{BE}$  should always be taken as 0.7 V, unless mention.

If we see the figure,  $I_B$  at the Q point is  $25 \mu\text{A}$ .

$$\text{Hence } R_B = 772 \text{ k}\Omega$$


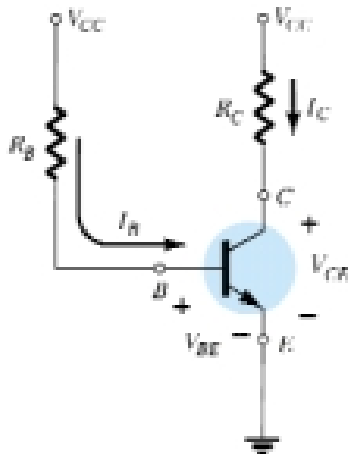


Figure of fixed bias configuration from Boylestad.

2. Find the emitter current.

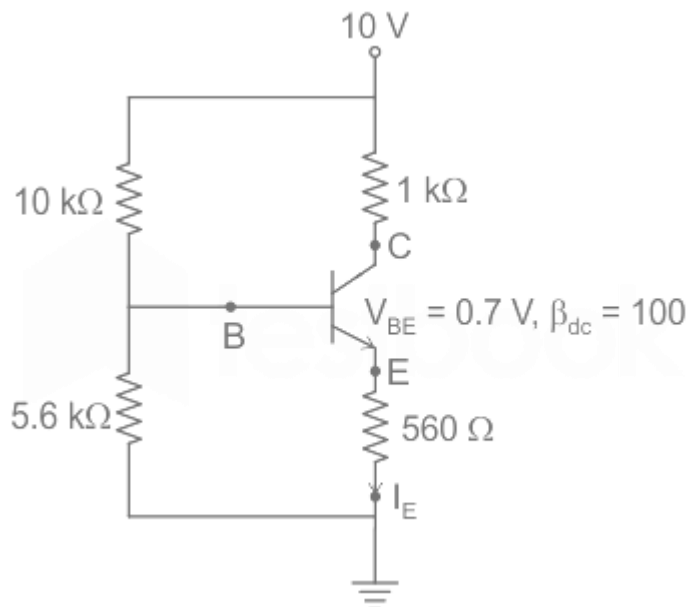


**Answer:** 5 mA

Hint: Calculate  $V_{th} = V_B = 10\text{ V} * (10/10+5.6)$  - voltage divider rule at point B

Apply KVL  $V_B - V_{BE} - I_E R_E = 0$  this will give  $I_E = 5\text{ mA}$

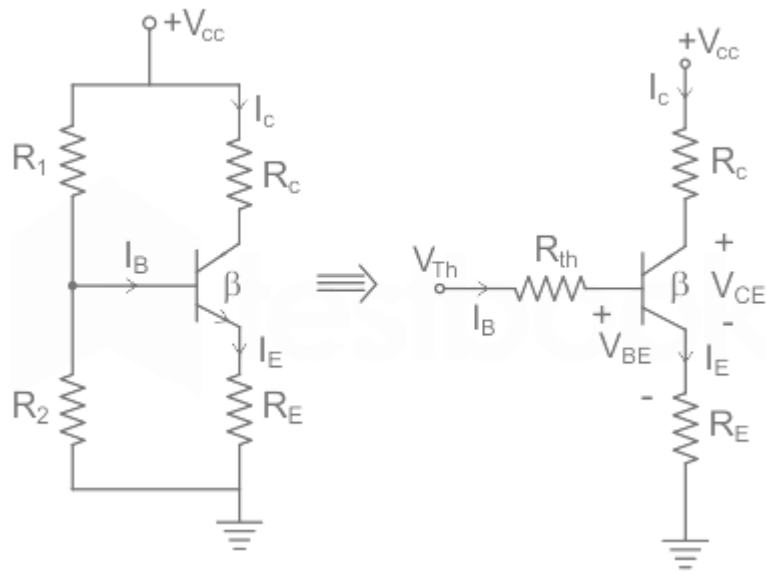3. Consider voltage divider circuit:  $R_1 = 50\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ ,  $\beta = 100$ ,  $V_{CC} = 12\text{ V}$  and  $V_{BE} = 0.7\text{ V}$ . Find out the  $I_C$ ,



**Answer:** 1.2 mA

Calculate  $V_{th}$  and  $R_{th}$ .

$$V_{th} = 12 * (10/10+50) = 2 \text{ V and } R_{th} = R_1 || R_2 = 25/3 \text{ k}\Omega$$

Now apply KVL,

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$


$$\text{Put, } I_E = I_B (\beta + 1),$$

$$I_B = 11.9 \text{ }\mu\text{A (approx. value 12)}$$

$$\text{We know, } I_C = \beta * I_B$$

$$\text{Hence, } I_C = 1.19 \text{ mA (approx. value 1.2)}$$

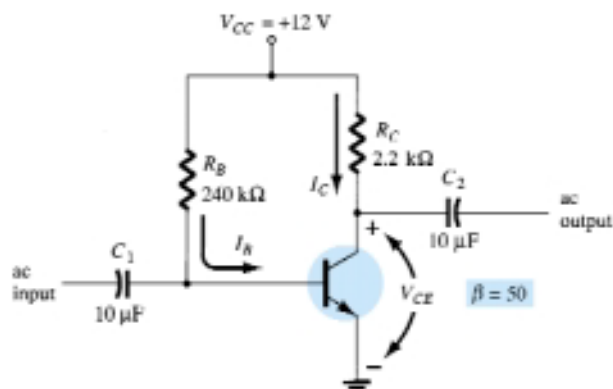
4. **For the fixed bias network, find out  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_B$ ,  $V_C$ , and  $V_{BC}$ . What happen if  $\beta$  increases to 100.**



**Answer:** Please see solved example 4.1 and 4.5 in the Boylestad book. Already discussed in the class.

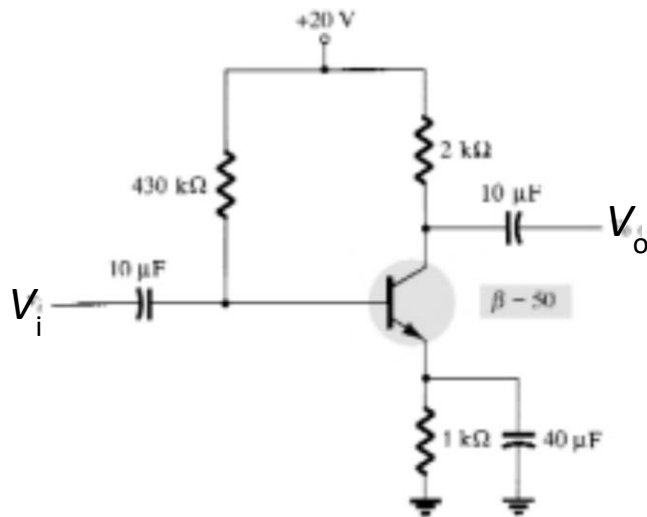
5. **For the emitter bias network, determine:**

$I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_C$ ,  $V_E$ ,  $V_B$ ,  $V_{BC}$ . What happen if  $\beta$  is increased to 100.




**Answer:** Please see solved example 4.4 and 4.5 in Boylestad book. Already discussed in the class.

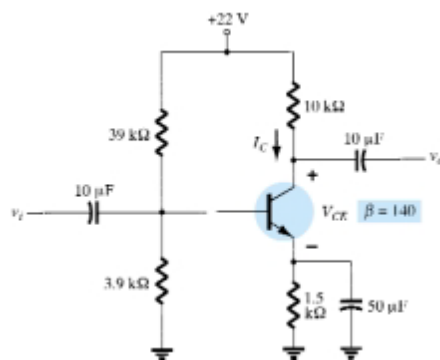6. In the voltage divider circuit, find out  $I_C$  and  $V_{CE}$ . Also, find out what happen if  $\beta$  is decreases to 70.



**Answer:** Please see solved example 4.7 and 4.9. Already discussed in the class using beta value 50 and 100.

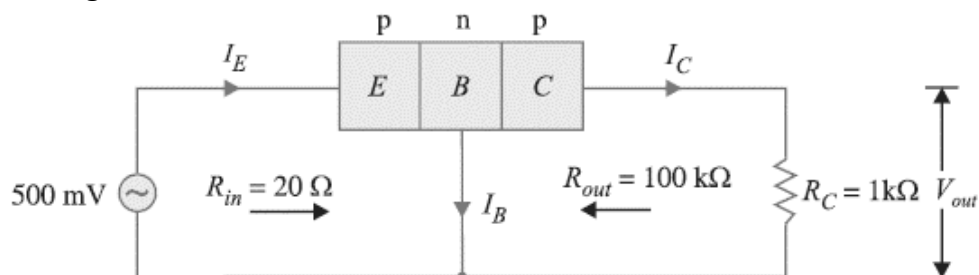7. Consider the CB configuration, if  $\alpha$  is nearly one, find the voltage gain for the following circuit:



**Answer: 50**


Here,  $I_E = 500 \text{ mV} / 20 \Omega = 25 \text{ mA}$

$I_C = I_E$

$V_{\text{out}} = 25 \text{ mA} * 1 \text{ k} \Omega = 25 \text{ V}$

Gain =  $25 \text{ V} / 500 \text{ mV} = 50$

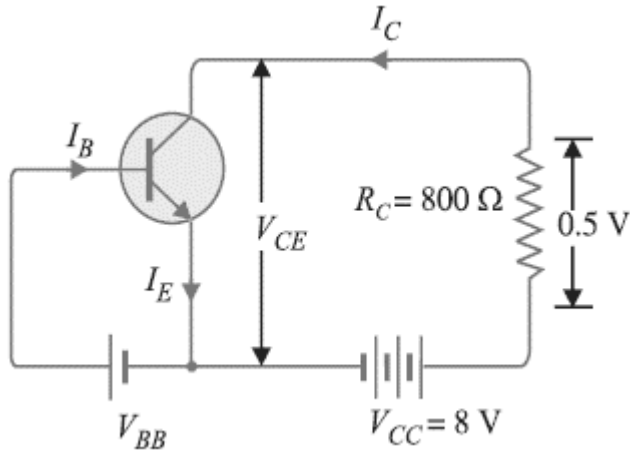8. Find base current and  $V_{CE}$ , if  $\alpha = 0.96$



**Answer: 26  $\mu\text{A}$  and 7.5 V**

$V_{CE} = V_{CC} - I_C R_C = 8 - 0.5 = 7.5 \text{ V}$

$I_C = 0.5 \text{ V} / R_C = 0.625 \text{ mA}$

$\beta = 0.96 / (1 - 0.96) = 24$

$I_B = 0.625 / 24 = 0.026 \text{ mA}$

9. The collector leakage current in a transistor is  $300 \mu\text{A}$  in CE arrangement. If the transistor is connected in CB arrangement, what will be the leakage current? Given that  $\beta = 120$ .

**Answer: 2.4  $\mu\text{A}$**


Here, the leakage current in CE and CB configuration is  $I_{CEO}$  and  $I_{CBO}$ .

$I_{CEO} = I_{CBO} / (1 - \alpha)$

$\alpha = 0.992$

$I_{CBO} = 300 * 0.08 = 2.4 \mu\text{A}$

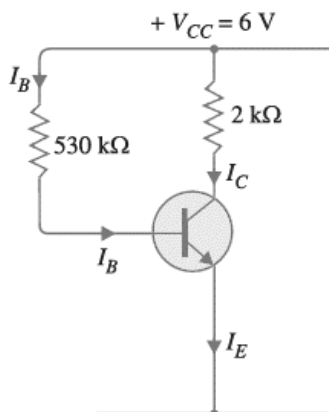10. Consider the fixed bias configuration:



**Draw the dc load line. If  $V_{BE} = 0.7 \text{ V}$  and  $\beta=100$ , find operating point i.e.,  $I_C$  and  $V_{CE}$ .**

**Answer:** To draw DC load line, we need to determine  $I_{C,sat} = V_{CC}/R_C = 6 \text{ V} / 2 \text{ k}\Omega = 3 \text{ mA}$

Operating point: Using KVL

$$6 - 530 \text{ k}\Omega \cdot I_B - 0.7 = 0$$

$$I_B = 10 \text{ }\mu\text{A}$$

$$I_C = 1 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 4 \text{ V}$$

